

Solar charging solution provides narrow-voltage DC/DC system bus for multicell-battery applications

By Wang Li, Battery Power Applications Engineer,
and Michael Day, Power Applications Manager

Introduction

Solar-powered systems typically must operate from a very wide input-voltage range due to the large variations in a solar panel's output voltage. This wide operating range limits the system's ability to consume maximum power from the solar cell under all light conditions. The ideal solar charging application operates the solar cell at its maximum power point (MPP) while simultaneously limiting the input-voltage range of the system. This goal is achieved by integrating a narrow-voltage DC/DC (NVDC) battery-charging architecture with a solar-charger design. The narrow voltage range for the system power bus provides higher system efficiency, minimizing battery charging times and extending battery run times.¹ This article shows the NVDC charging architecture in a solar charging application and introduces a circuit that provides acceptable charger operation under several operating conditions, such as battery overtemperature, a discharged battery, a fully charged battery, and a system-current overload.

Conventional charger topology


Figure 1 shows a conventional charger topology used with high-power switching chargers. Notebook charging is a typical application for this topology. One drawback is the system's wide operating voltage range, which requires more expensive, less efficient power supplies to generate the

power rails for the downstream circuitry.¹ The system voltage ranges from the highest AC adapter voltage (typically 22 V for a lightly loaded adapter) to the lowest battery voltage, which is 9 V for a 3S2P laptop battery pack. (3S2P is an abbreviation for three batteries in series with two of these series connections in parallel.) When the AC adapter is present, the power-path-selector MOSFETs (Q1 and Q2) turn on, and the battery MOSFET (Q3) turns off. The AC adapter voltage is applied to both the system voltage and the battery charger's input, delivering power to both circuits simultaneously. If the AC adapter voltage drops due to a brownout, an overcurrent condition, or unplugging the adapter, Q1 and Q2 turn off to prevent battery power from flowing backwards into the adapter. Q3 turns on and connects the battery-pack voltage directly to the system. In this way, the system is always supplied with power—either from the adapter or the battery.

Requirements of a solar-powered charger

The battery-charger architecture in Figure 1 is acceptable for systems that use an AC adapter, but it is not ideal for solar charging applications because there is no way to limit the input current. To keep the solar cell always operating at its MPP, which will minimize battery charge time and the solar cell's size and cost, the charger needs a current-limiting mechanism. Unlike a conventional AC wall adapter,

Figure 1. Conventional charger topology

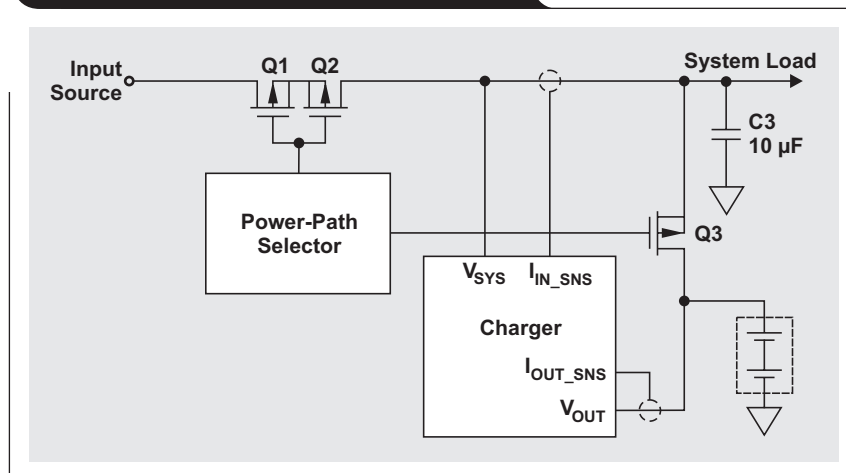


a solar cell should be operated with very tight control over its load current. Figure 2 shows the V-I characteristics of a typical solar cell under one light condition and helps explain this concept. The solid line represents the output current of the solar panel as its voltage varies, while the dashed line represents the output power. Because the panel's voltage drops as the current it delivers increases, an MPP is created at a specific voltage and current. A solar cell's MPP varies with different light conditions and temperatures. If very little charging and system current are required, the solar cell may operate at Point A in Figure 2, which is below its MPP. The solar cell delivers less than its maximum power, which is acceptable because the system is getting the power it needs. However, if the battery charge current or system power requirements increase, the charger pulls more current and the solar cell operates at Point B in Figure 2. At Point B, the solar cell's output current has increased, but the actual delivered power has gone down because of the drop in voltage. With reduced power from the solar cell, it takes longer to charge the battery. A well-designed solar-cell charger should contain circuitry that separates the solar cell from the system as well as circuitry that controls the solar cell's total current so the cell can be operated at its MPP. This combination of circuitry can fully utilize the solar cell's available power, resulting in a less expensive system because the designer does not have to oversize the solar cell to meet charging requirements.

Basics of maximum-power-point tracking

Solar-cell chargers include special circuitry called maximum-power-point tracking (MPPT) circuitry that prevents the charger from consuming more than the solar cell's maximum power. This is typically implemented by setting the minimum operating voltage that corresponds with the solar cell's MPP.

A design using the solar cell in Figure 2 allows the charger and system to draw any current from the solar cell as long as the solar cell's voltage remains above V_{MPP} . When the current increases to the point where the voltage drops to V_{MPP} , a special control loop in the charger takes over and regulates the total current from the solar cell to maintain the solar cell's voltage at V_{MPP} . At this operating point, the solar cell delivers its maximum power. Any power not required for the system load is used to charge the battery. This voltage-based MPPT circuitry is fairly accurate at providing maximum power, even with varying solar-cell illumination levels. Although reduced light lowers the solar cell's maximum power and current capability, the

Figure 2. Solar panel's V-I curve and output-power curve

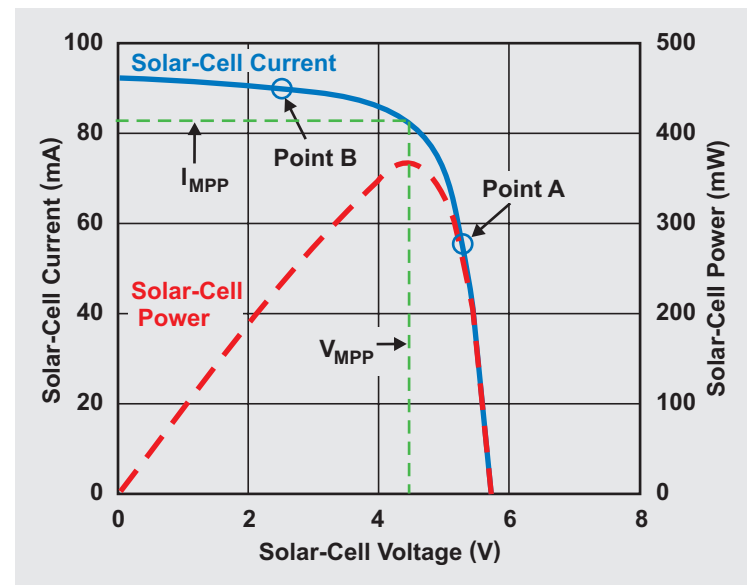


MPP is still achieved at approximately the same voltage.² Voltage-based MPPT circuitry typically consists of only two resistors external to the battery charger.³ All other circuitry is integrated into the charger IC itself. A solar cell's V_{MPP} does vary significantly with temperature. If desired, additional circuitry can be added to track a solar cell's V_{MPP} change with temperature. Tracking MPP over temperature can reduce charging times by 40%.⁴

Adding NVDC charging architecture

Figure 3 shows how a narrow-voltage DC/DC (NVDC) charging architecture can separate the solar cell from the system. Rather than being connected to the solar cell via

Figure 3. NVDC architecture with MPPT circuitry

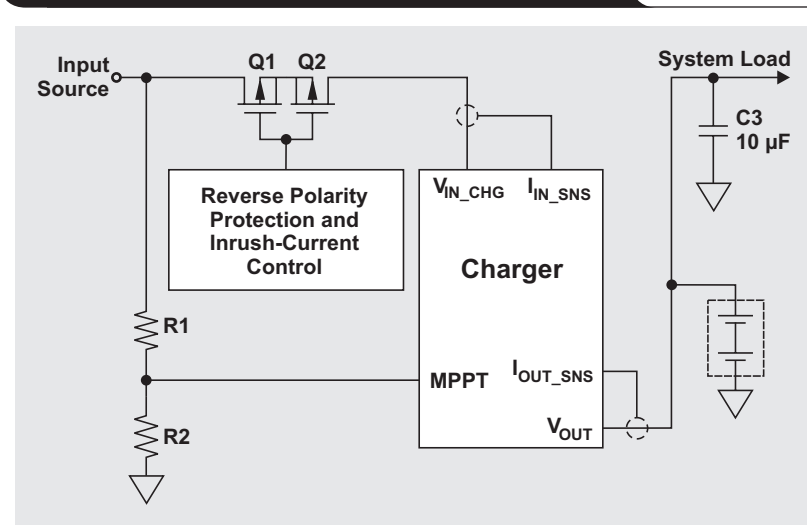

the power-path-selector FETs, the system is connected directly to the battery. The system voltage is now equal to the battery voltage, regardless of the input voltage of the adapter or solar cell. The narrow operating voltage allows the designer to optimize the system power supplies for size, cost, and efficiency.¹ It also eliminates the need for the battery FET. The NVDC architecture is useful for solar charging because it routes all current through the charger. This allows the MPPT circuitry to effectively control the total current from the solar cell and maintain operation at the maximum rated power.

Connecting the system directly to the battery as in Figure 3 has significant advantages, but it also has disadvantages under certain operating conditions that should be considered. These conditions are as follows:

1. When the battery voltage is lower than the battery's precharge voltage, the battery current must be limited to the precharge current, which may not be sufficient to operate the system.
2. When the battery temperature is outside the allowable range for charging, the charger must disable charging, which also disables the system's power.
3. When the battery is fully charged, it should be disconnected from the charging source to extend battery life, but the system should remain on.

All of these conditions can be addressed with the addition of FETs Q4 and Q5 to the NVDC architecture (see Figure 4). A gas gauge or a host controller monitors voltages, current, and battery temperature and uses these inputs to control the FETs, which connect or disconnect the battery to or from the charger depending on the operating conditions. The host can be as complicated as a microprocessor with analog-to-digital converters that continuously monitors operating conditions and adjusts charger performance based on the system's needs, or it can be

simple, discrete circuitry that monitors only battery voltage and temperature.


A deeply discharged battery requires preconditioning prior to being charged. Typical Lithium-Ion (Li-Ion) batteries require the charger to apply a precharge current that is 1/10 of the fast-charge current until the battery voltage rises above a specific voltage, typically 3 V/cell. When the host detects a battery voltage that is less than the specified precharge voltage ($V_{BAT} < V_{PRECHG}$), it turns Q5 on and provides a precharge current through R_{PRECHG} . The value of R_{PRECHG} is chosen to provide the maximum allowable precharge current when the battery voltage is fully discharged. In this operating mode, the system is effectively isolated from the battery voltage, which allows the charger to maintain the NVDC regulation voltage even with a discharged battery. When the battery voltage increases above the precharge voltage, the host turns Q5 off and Q4 on, effectively shorting the battery and the system together. The battery's charge current increases to the charger's maximum output current minus the current into the system. If the system current exceeds the charger's fast-charge current, the battery enters supplement mode where current flows out of the battery to the system.

If the host detects an over- or undertemperature fault condition, it turns off both Q4 and Q5. This stops the battery charging while still allowing the charger to power the system. The host can also turn Q4 and Q5 off when the battery reaches its full-charge voltage to increase battery life. Detailed information on the battery-disconnect circuitry can be found in Reference 5.

Conclusion

The NVDC charger architecture coupled with MPPT and the battery-disconnect circuitry provides several advantages over standard charging architectures. It intelligently connects and disconnects the battery from the system

Figure 4. NVDC architecture with battery-disconnect circuitry

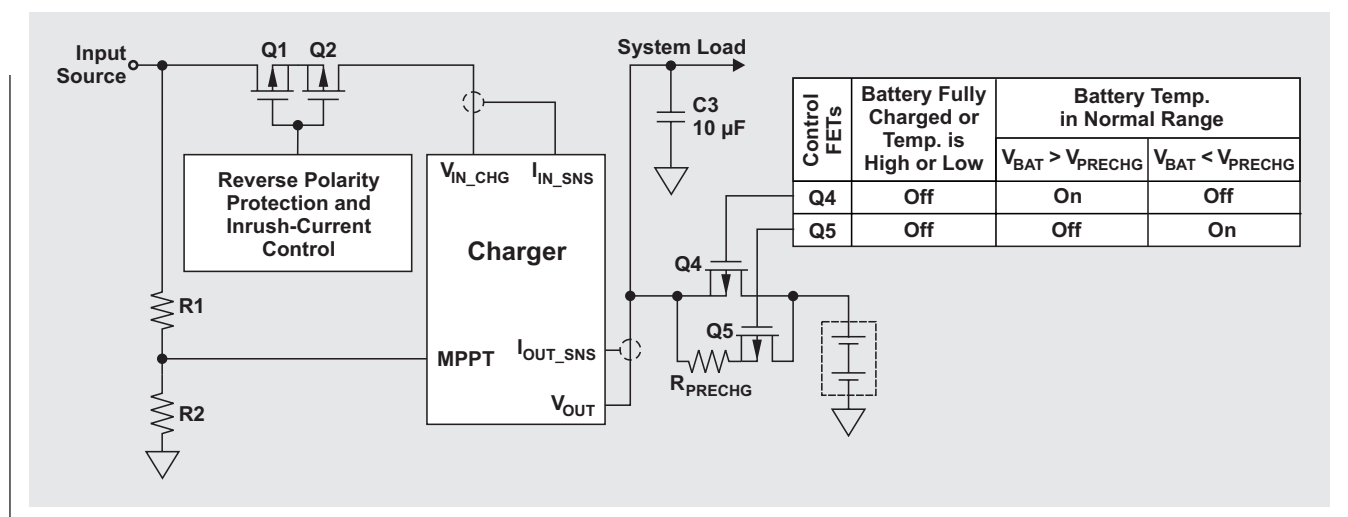

under the appropriate operating conditions, allowing the designer to optimize the solar panel's output power for the system's needs. The charger also provides a narrow system operating voltage, which optimizes efficiency and extends battery life.

References

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace “litnumber” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Xiaoguo Liang, Gnanavel Jayakanthan, and Meng Wang, “Design considerations for narrow Vdc based power delivery architecture in mobile computing systems,” in <i>Proc. Applied Power Electronics Conference and Exposition (APEC)</i> , Palm Springs, CA, 2010, pp. 794–800 [Online]. Available: http://ieeexplore.ieee.org —	

Document Title	TI Lit. #
2. Lokesh Ghulyani, “Simple MPPT-based lead acid charger using bq2031,” Application Report.	SLVA378
3. “Synchronous switch-mode battery charge controller for solar power with maximum power point tracking,” bq24650 Datasheet . . .	SLUSA75
4. Jared Casey, “Maximum power point tracking with the bq24650 charger,” Application Report.	SLUA586
5. Wang Li, “A discrete narrow voltage DC/DC (NVDC) charger solution for multi-cell batteries,” Application Report	SLUA620

Related Web sites

power.ti.com
www.ti.com/product/bq2031
www.ti.com/product/bq24650

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E is a trademark of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated